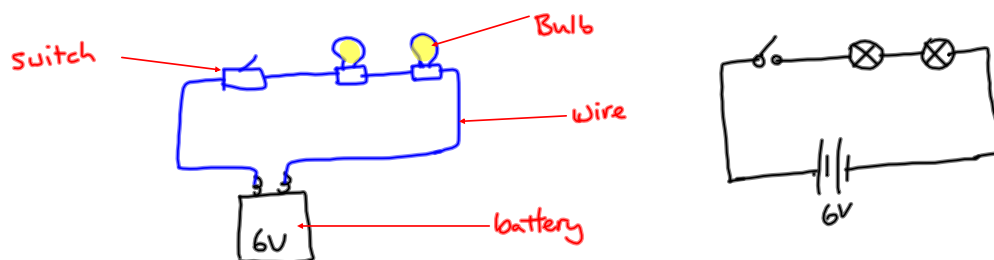


## Current Electricity. Parallel and Series Circuits

---

### Parallel Circuit



- Comment :
- If one light is broken neither light up.
  - The more bulbs in the circuit the dimmer the light from each bulb.
- 

### Series Circuit



- Comment :
- If light is broken the other still lights up.
  - The brightness of each bulb is not affected by the no. of bulbs.